



EXPERIMENT ON VERIFICATION OF KIRCHHOFF'S CURRENT LAW (KCL)



AIM

To experimentally verify Kirchhoff's Current Law



OBJECTIVES


At the end of this lesson, you should be able to:

- State Kirchhoff's Current Law (KCL) for electric circuits.
- Apply Kirchhoff's current law at node (or junction) points in an electric circuit.



APPARATUS

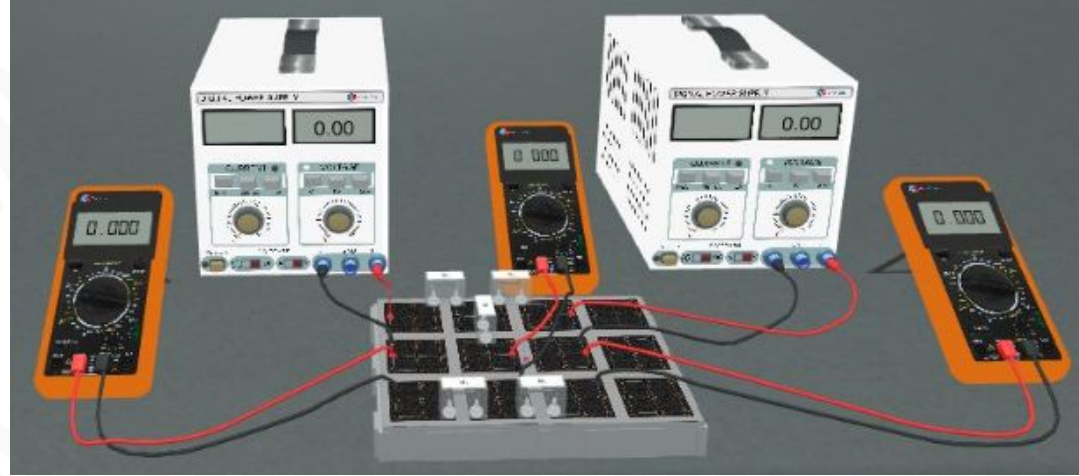- Breadboard.
- Two DC power supplies.
- Five variable resistors.
- Three ammeters.
- Connection cables.





THEORY

Analysing electric circuits depends on two basic laws that were developed by the Russian scientist Justaff Kirchhoff in 1845.

- Kirchhoff's First Law (or current law) KCL
- Kirchhoff's Second Law (or Voltage law) KVL



KIRCHHOFF'S CURRENT LAW (KCL)

KCL is based on the principle of conservation of charge.

It states that:


The sum of currents that enter the junction equals the sum of currents that leave the junction.

Or

The sum of all currents entering and leaving a junction point in a circuit is zero, with currents entering the junction considered positive and those leaving the junction considered negative.

$$\sum I_{in} = \sum I_{out}$$

$$\sum I = 0$$

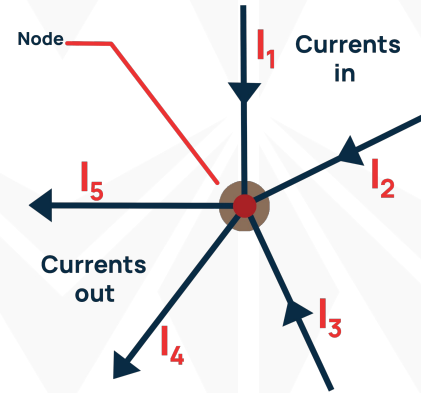

$$I_1 + I_2 + I_3 + (-I_4 - I_5) = 0$$






THEORY

At node b in the figure,

$$I_1 + I_2 = I_3 \quad (1)$$
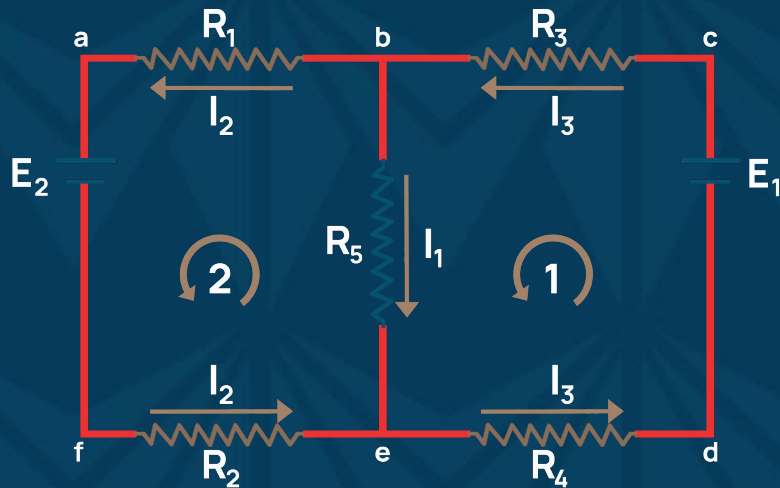
$$-I_1 - I_2 + I_3 = 0 \quad (\text{Current Entering is +ve})$$





MID-LESSON QUESTIONS

Q1: Explain Kirchhoff's Current Law (KCL) in your own words.

Q2: You have a circuit with three branches connected at a junction. If you measure a current of 2 amperes entering the junction from one branch, how much total current should be leaving the junction?



MID-LESSON ANSWERS


A1: Kirchhoff's Current Law (KCL) states that the total current entering a junction or node in an electrical circuit must be equal to the total current leaving that junction or node. In other words, the sum of currents at any point in a circuit is conserved, signifying the principle of charge conservation.

A2: According to Kirchhoff's Current Law (KCL), if 2 amperes of current are entering the junction, the total current leaving the junction must also be 2 amperes. KCL ensures that the conservation of charge is maintained at the junction, so the sum of currents entering and leaving must be the same.



PROCEDURE


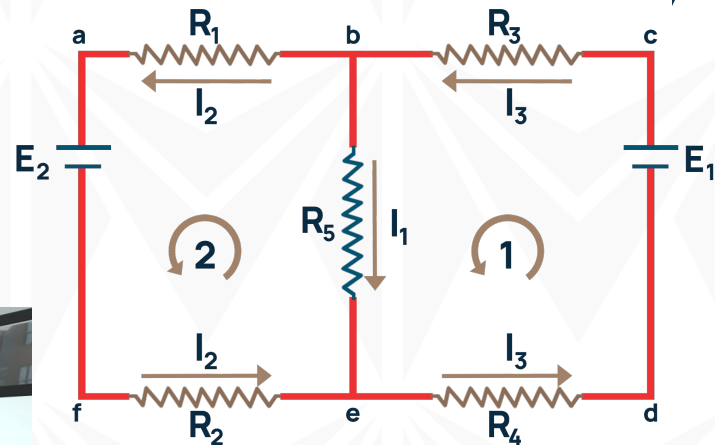
1. Select the values of R_1 through R_5 and connect the circuit as shown.







PROCEDURE

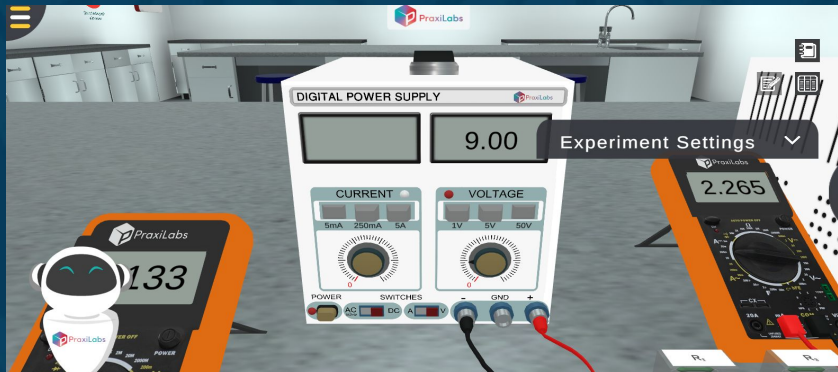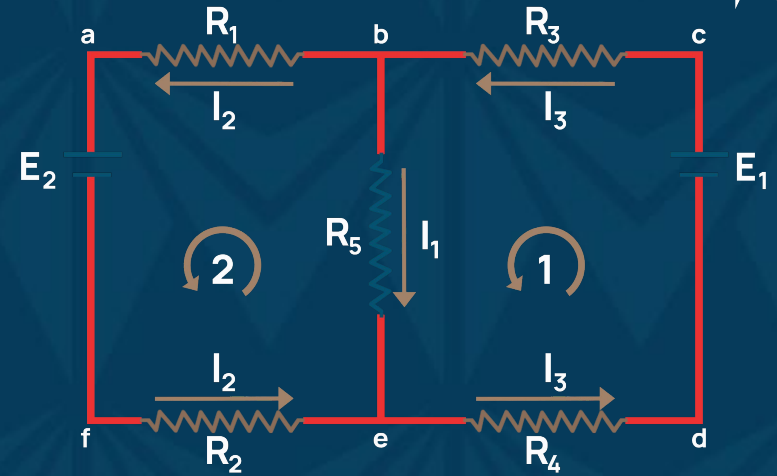2. Select the maximum output voltage of both DC power supplies to be 50 V by pressing the 50 V button above the voltage dial.
3. Adjust the emfs of both supplies to 9 V using the voltage dial knob.





PROCEDURE

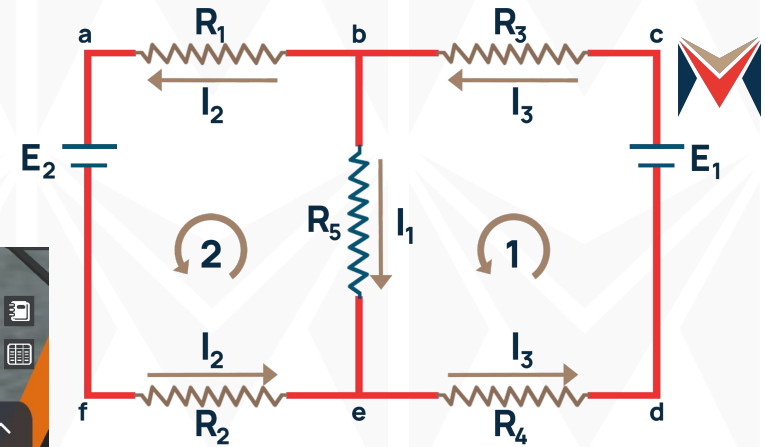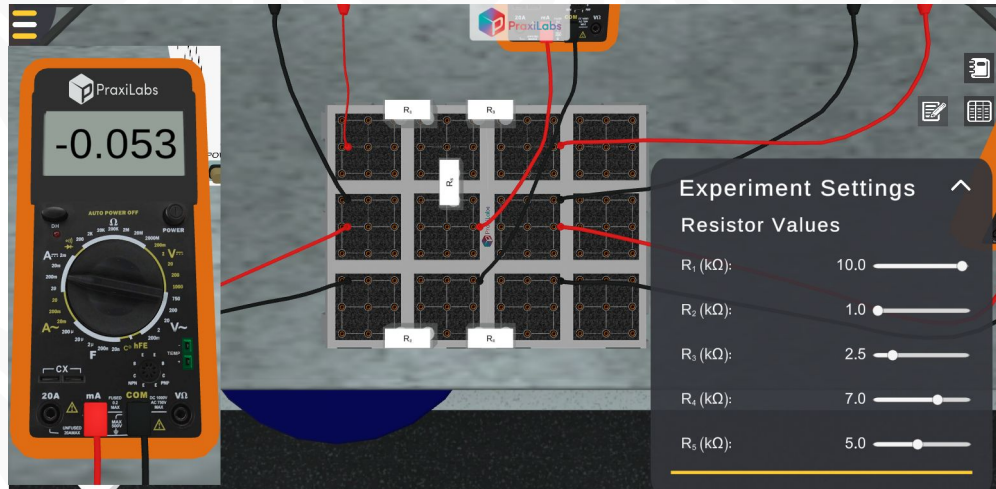

4. Click the Record button to record the readings of the three ammeters.
5. Increase the EMF E_2 at regular intervals (3 V) and repeat step 4



PROCEDURE

6. Save the Excel file you downloaded

R_1 (k Ω)	R_2 (k Ω)	R_3 (k Ω)	R_4 (k Ω)	R_5 (k Ω)	E_2 (V)	E_1 (V)	I_1 (mA)	I_2 (mA)	I_3 (mA)	$I_{3\text{-compute}}$ I_d (mA)
10	1	2.5	7	5	9	9	0.895	-0.416	0.479	
10	1	2.5	7	5	9	12	1.055	-0.344	0.711	
10	1	2.5	7	5	9	15	1.215	-0.271	0.944	




DATA ANALYSIS

R_1 (k Ω)	R_2 (k Ω)	R_3 (k Ω)	R_4 (k Ω)	R_5 (k Ω)	E_2 (V)	E_1 (V)	I_1 (mA)	I_2 (mA)	I_3 (mA)	$I_{3\text{-compute}}$ I_d (mA)
10	1	2.5	7	5	9	9	0.895	-0.416	0.479	
10	1	2.5	7	5	9	12	1.055	-0.344	0.711	
10	1	2.5	7	5	9	15	1.215	-0.271	0.944	

1. Using the KVL equation $I_1 + I_2 = I_3$ (1)
1. Calculate the $I_{3\text{compound}}$ using I_1 and I_2 as shown in the table
1. Compare between the values calculated and the experimental values of I_3 and then comment on your results.



WALK THROUGH VIDEO

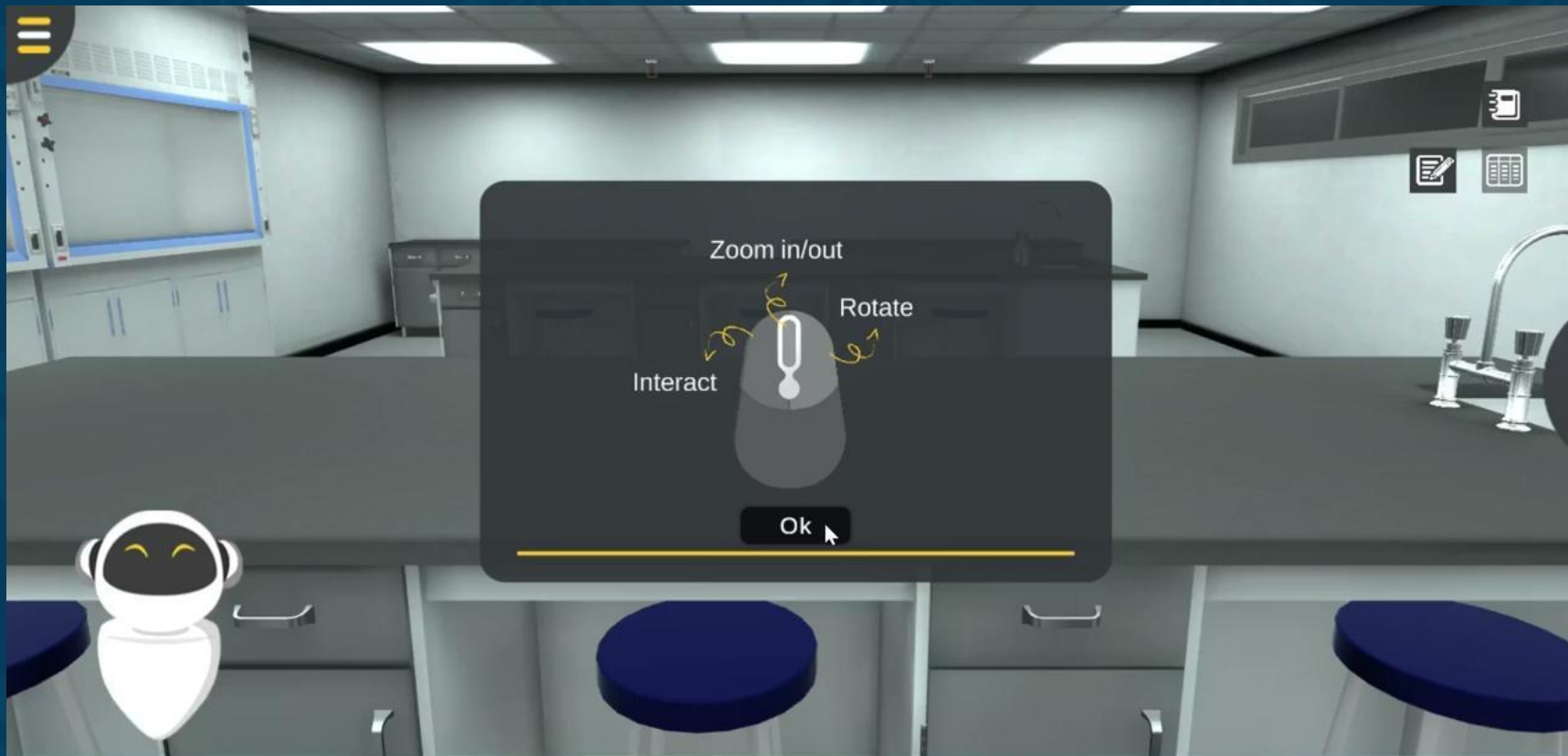



FURTHER READING

Bueche F. and Hecht E. Schaum's Easy Outlines - College Physics Crash Course. 2000 McGraw-Hill, USA.

Hernández-Hall, C. A., & Wilson, J. D. (2014). Physics Laboratory Experiments. Cengage Learning.

Sang, D., Hewlett, C., Jones, G., Field, S., & Styles, D. (2020). Cambridge International AS & A Level Physics Practical Workbook. Cambridge University Press.

Serway, R.A. and Jewett. J.W. (2014). Physics for Scientists and Engineers with Modern Physics, Ninth Edition. Physical Sciences: Mary Finch.



FURTHER READING

Shukla, R. K., & Srivastava, A. (2006). Practical Physics. New Age International (P) Limited, Publishers.

Young, H. D. (2012). Sears & Zemansky's college physics. 9th ed. Pearson Education, Inc.

<http://hyperphysics.phy-astr.gsu.edu>

<http://www.physicstutorials.org>



THANK
YOU